

Bachelor in Computer Applications

Course Title: **Digital Logics**

Code No: Semester: **1**

Full Marks: **60** Pass Marks: **24** Time: **3 hours**

Candidates are required to answer the questions in their own words as far as practicable.

Note: Group A (Multiple Choice Questions) is not available from the source. The paper begins with Group B.

Group B

1. Design a BCD-to Seven-segment decoder to display decimal numbers 1, 2 and 4.
2. What are the drawbacks of clocked RS flip flop? Explain the operation of a JK flip flop along with its characteristic table, characteristic equation circuit diagram and timing diagram.
3. Design a sequential circuit using JK flip-flop with the help of given state diagram.
4. Convert $(110.101)_2$ into binary and decimal number system.
5. Subtract $(739.57)_{10} - (78.35)_9$ using both 10's and 9's complement.
6. What is magnitude comparator? Design 2-bit magnitude comparator.
7. Define Half-subtractor with truth table and logic diagram.
8. What is decoder? Implement 8×1 MUX using 2×1 MUX.
9. Design and explain the operational characteristics of D flip flop.
10. Design Mod-5 synchronous counter using T- flip flop.
11. Draw a Serial-In Serial-Out Shift register and explain it.
12. Write short notes on: (Any two) a. BCD code b. Status Register c. Ring Counter